

Lab-2 Report

Implementation of CMOS logic gates

MIRIYALA PRANAY KAMAL
200030033

Aim: Identification of logic gates required for the given problems and implementation of the problem using the CMOS logic gates.

Components used:

1. IC HCF 4007 CMOS gates
2. Resistor array
3. DIP switches
4. LED displays
5. Breadboard
6. Power supply
7. Multimeter

Design Procedure:

Problem Statements:

1. A bulb in a staircase has two switches, one switch being at the ground floor and the other one at the first floor. The bulb can be turned ON and also can be turned OFF only if both the switches are at different states. Design the CMOS circuit for this logic.

Solution: **XOR Gate.**

2. A commercial building is powered by two renewable sources of energy – solar and wind. There are two alarms associated to both the generation stations that get HIGH if the power generation in any day is below the threshold values. Design the CMOS circuit that implements the logic of a third alarm which is switched ON if the generation by both the sources are below threshold on any given day.

Solution: **AND Gate.**

These XOR and AND gates can be implemented by using CMOS IC HCF 4007. The logic tables/Truth tables for these gates are:

AND GATE

INPUT 1	INPUT 2	OUTPUT
0	0	0
0	1	0
1	0	0
1	1	1

XOR GATE

INPUT 1	INPUT 2	OUTPUT
0	0	0
0	1	1
1	0	1
1	1	0

Other gates with CMOS:

NOR GATE

INPUT 1	INPUT 2	OUTPUT
0	0	1
0	1	0
1	0	0
1	1	0

NAND GATE

INPUT 1	INPUT 2	OUTPUT
0	0	1
0	1	1
1	0	1
1	1	0

XNOR GATE


INPUT 1	INPUT 2	OUTPUT
0	0	1
0	1	0
1	0	0
1	1	1

OR GATE


INPUT 1	INPUT 2	OUTPUT
0	0	0
0	1	1
1	0	1
1	1	1

Circuit diagram:


AND GATE USING CMOS

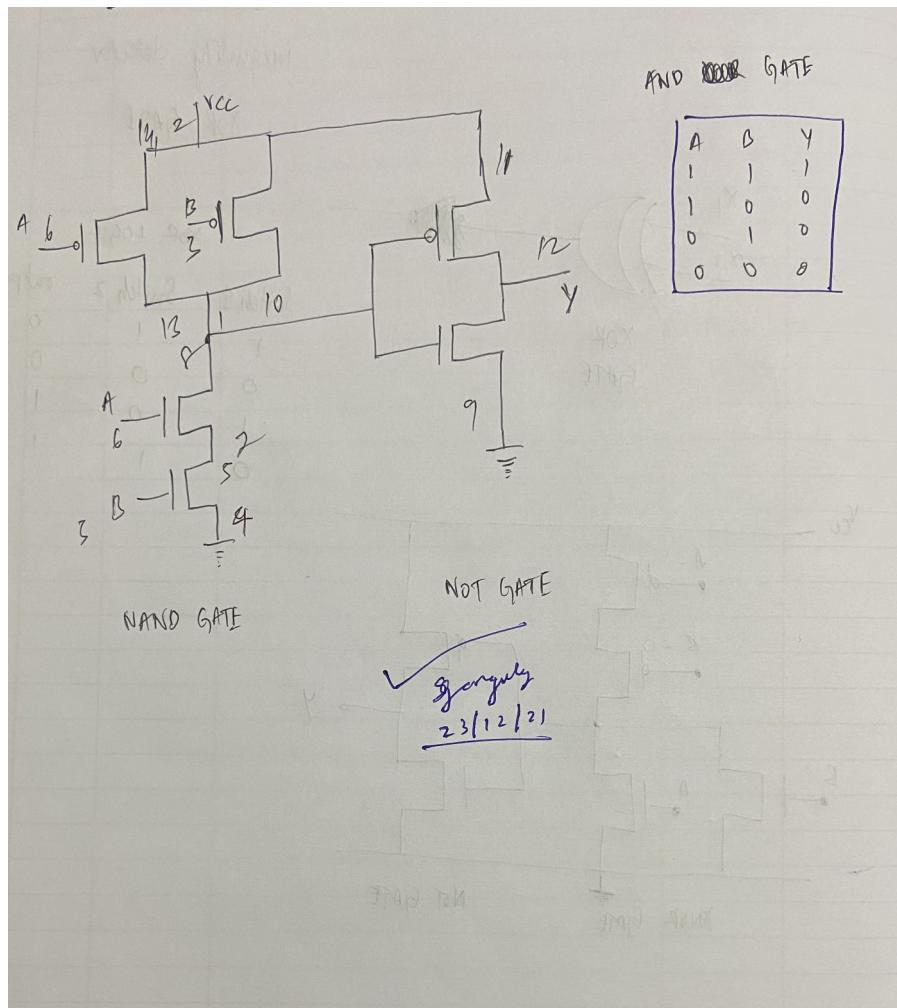


XOR GATE USING CMOS

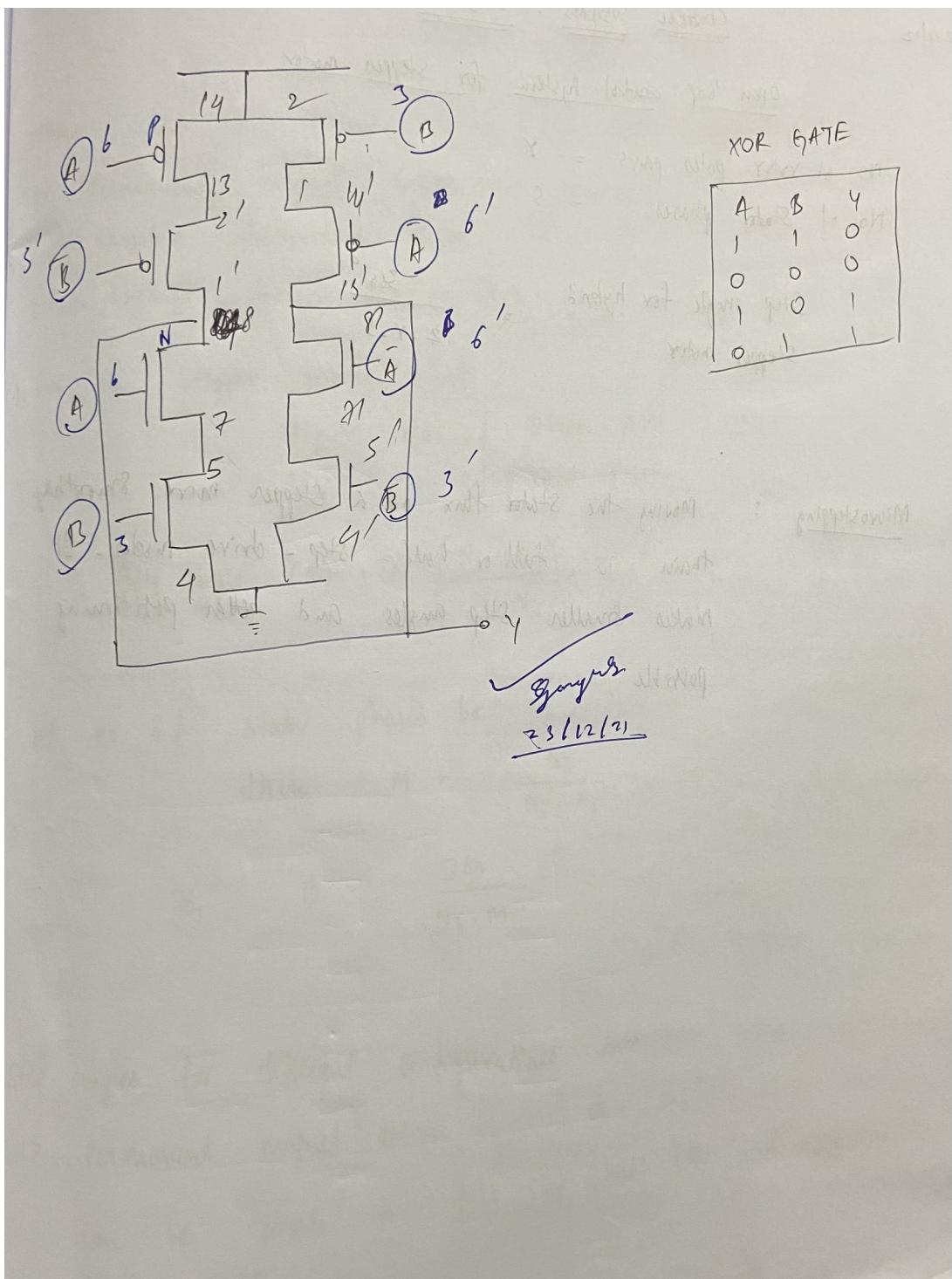


NOR GATE USING CMOS

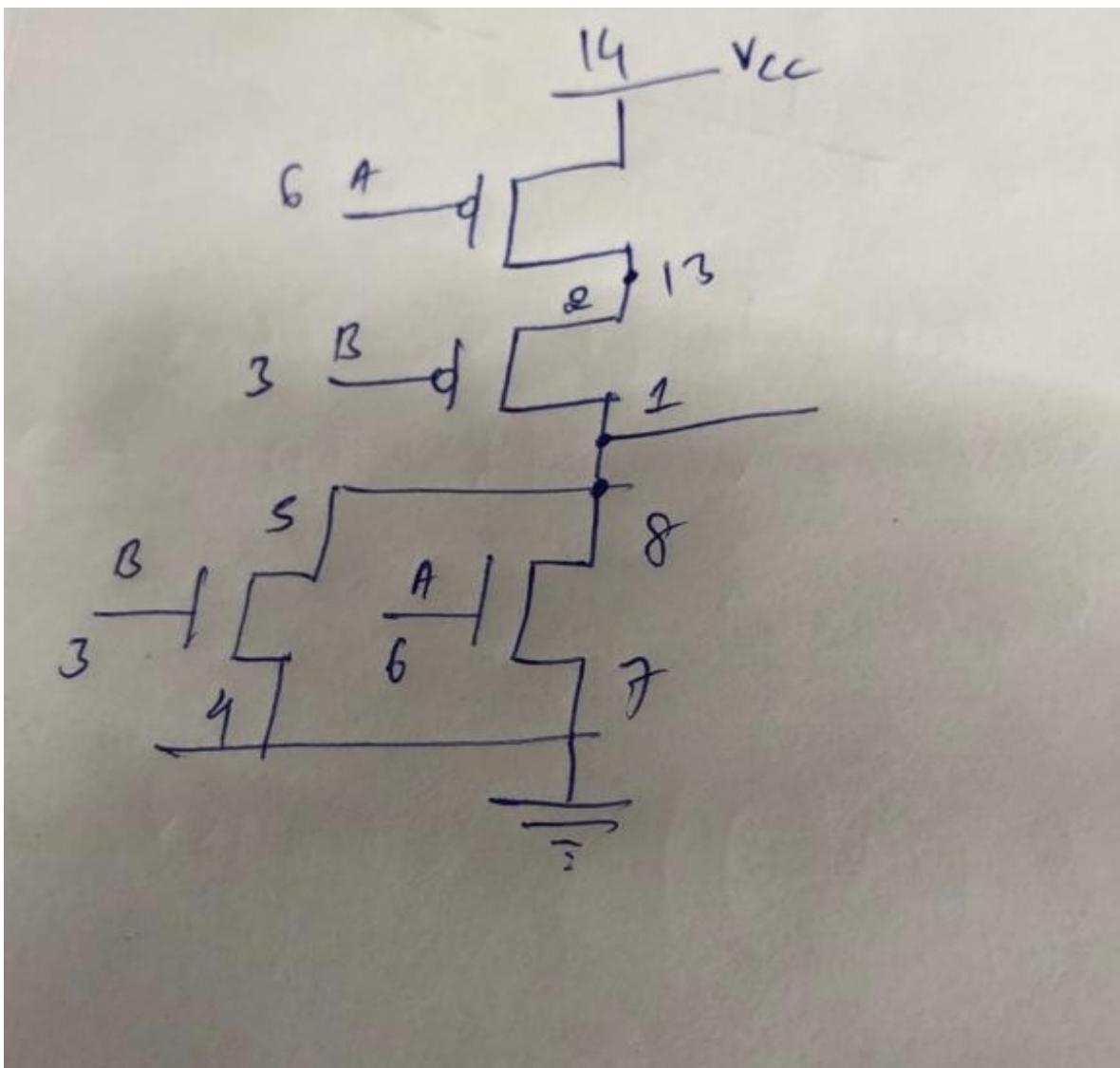

NAND GATE USING CMOS

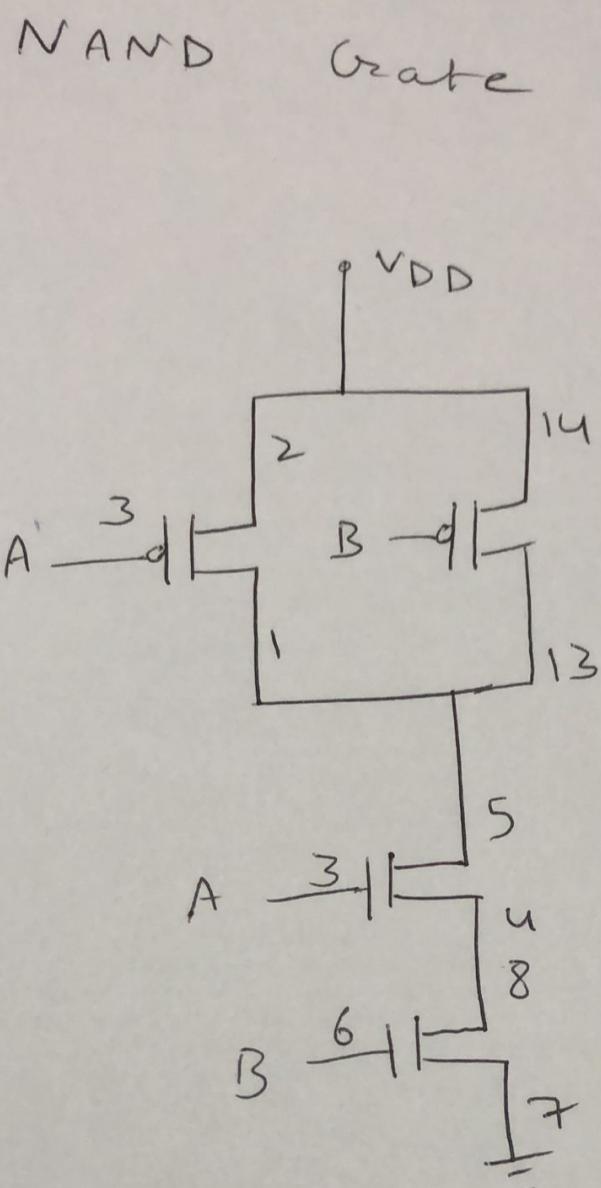


XNOR GATE USING CMOS

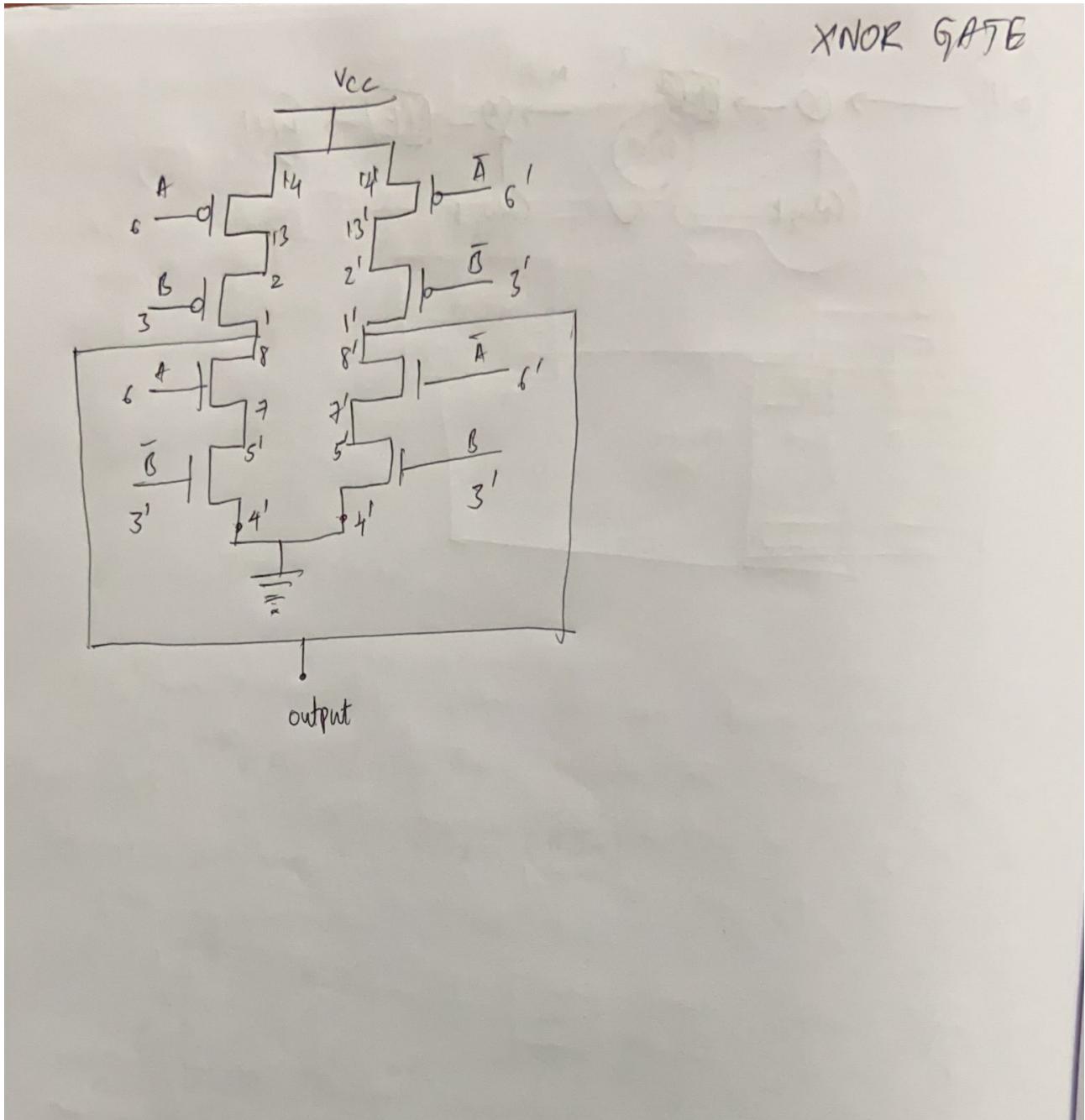





OR GATE USING CMOS

OR gate ;


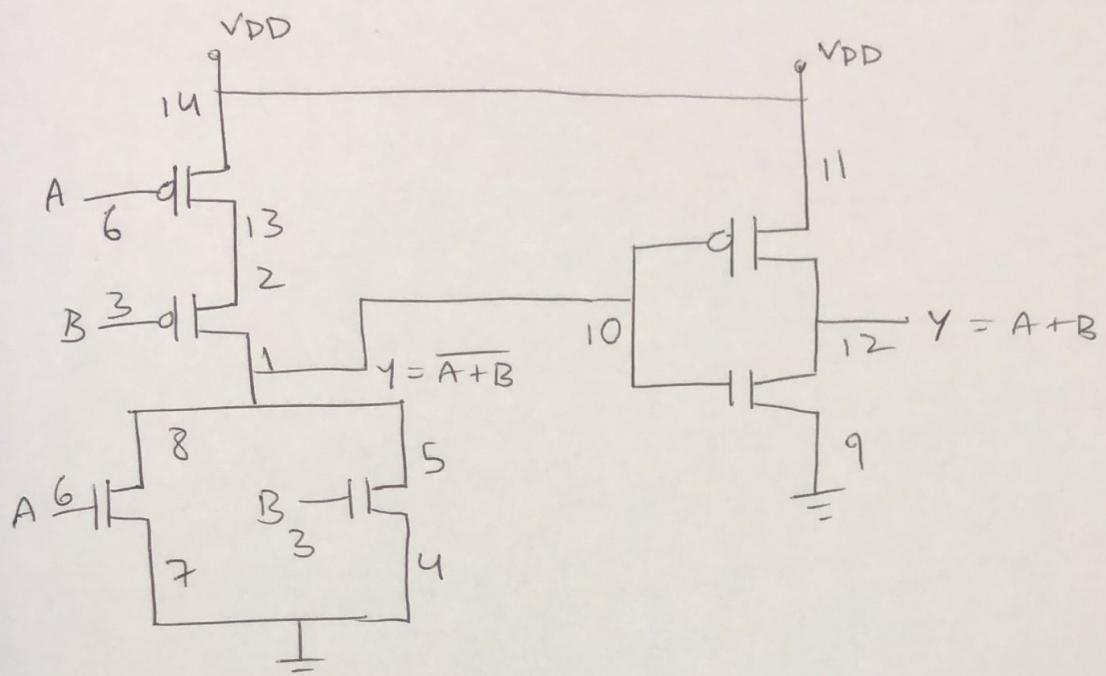


Circuit Snapshots:


1. XOR GATE

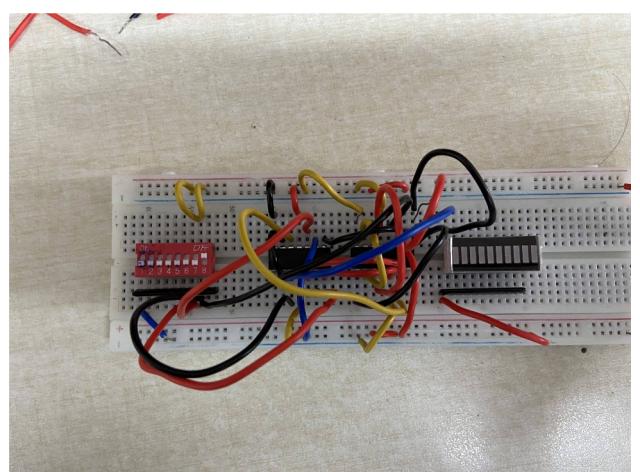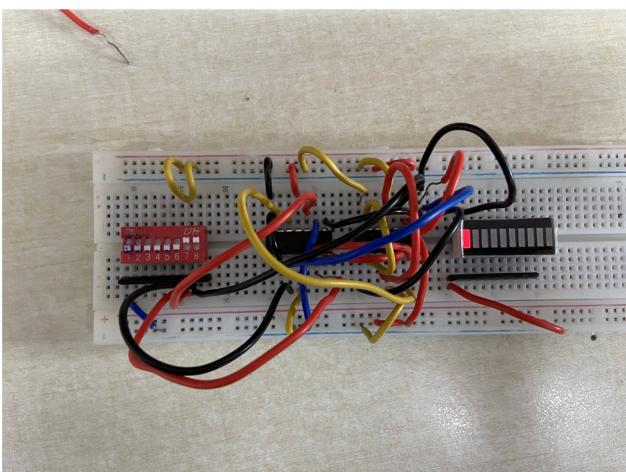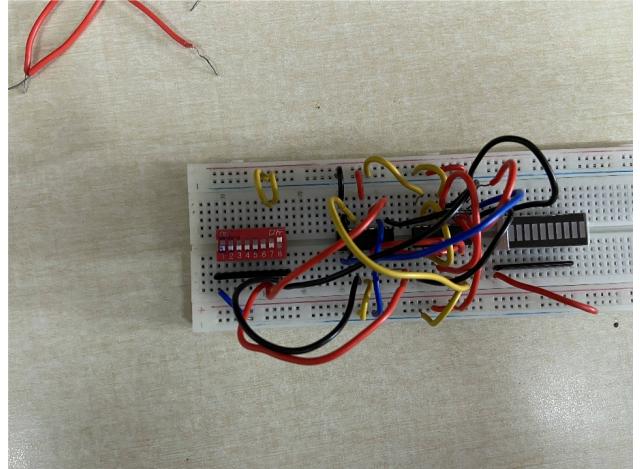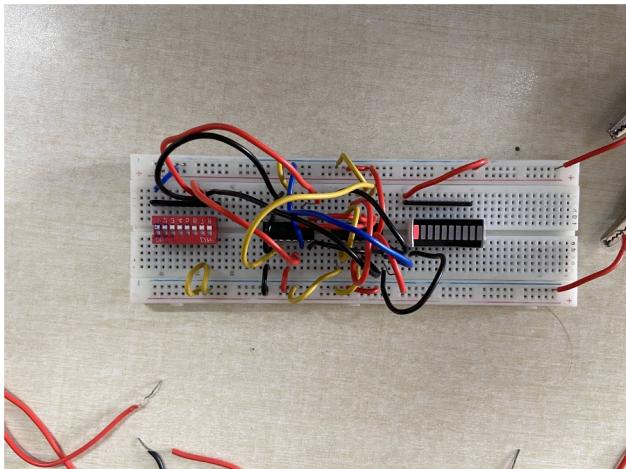


2. AND GATE

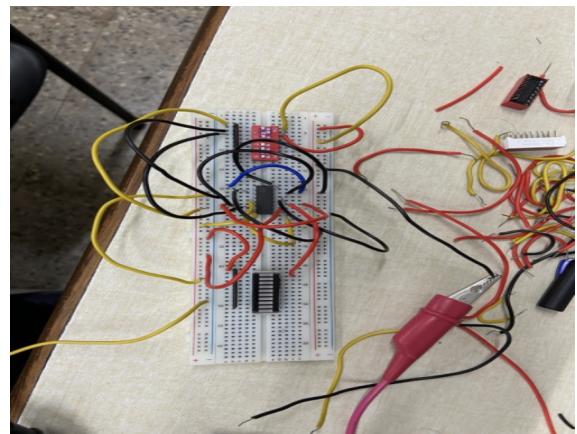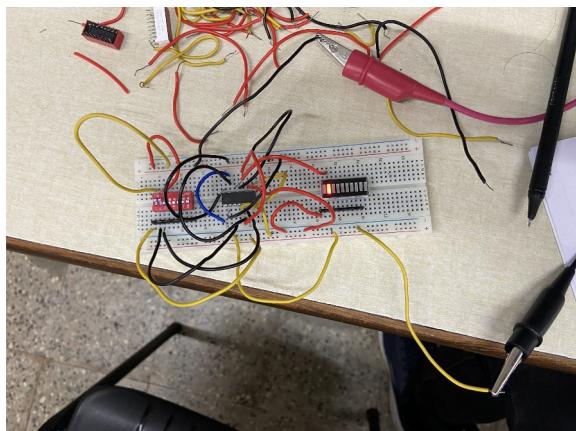

3. NOR GATE

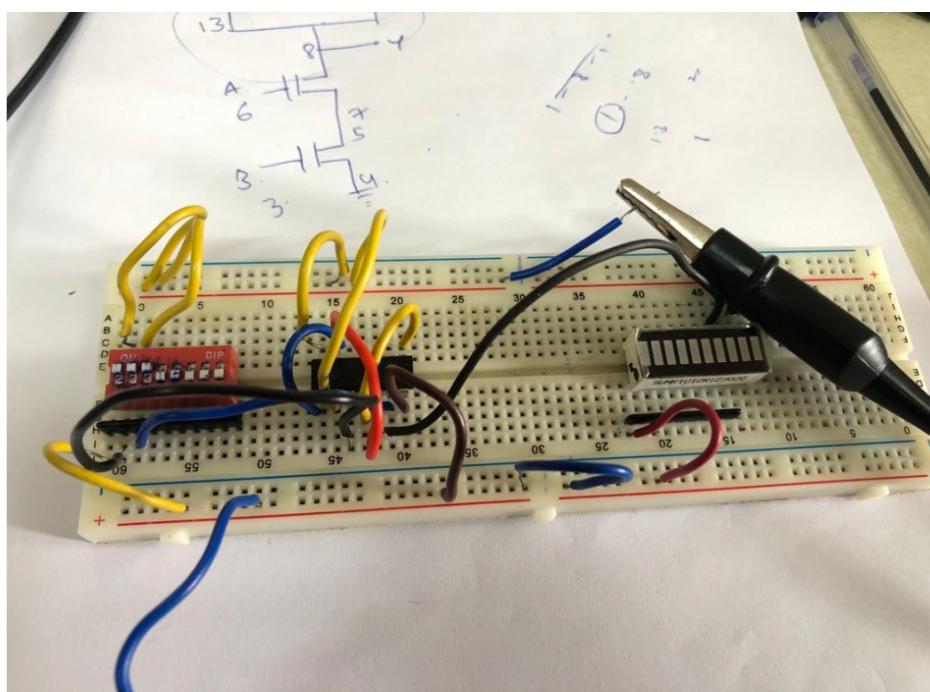

4. OR GATE

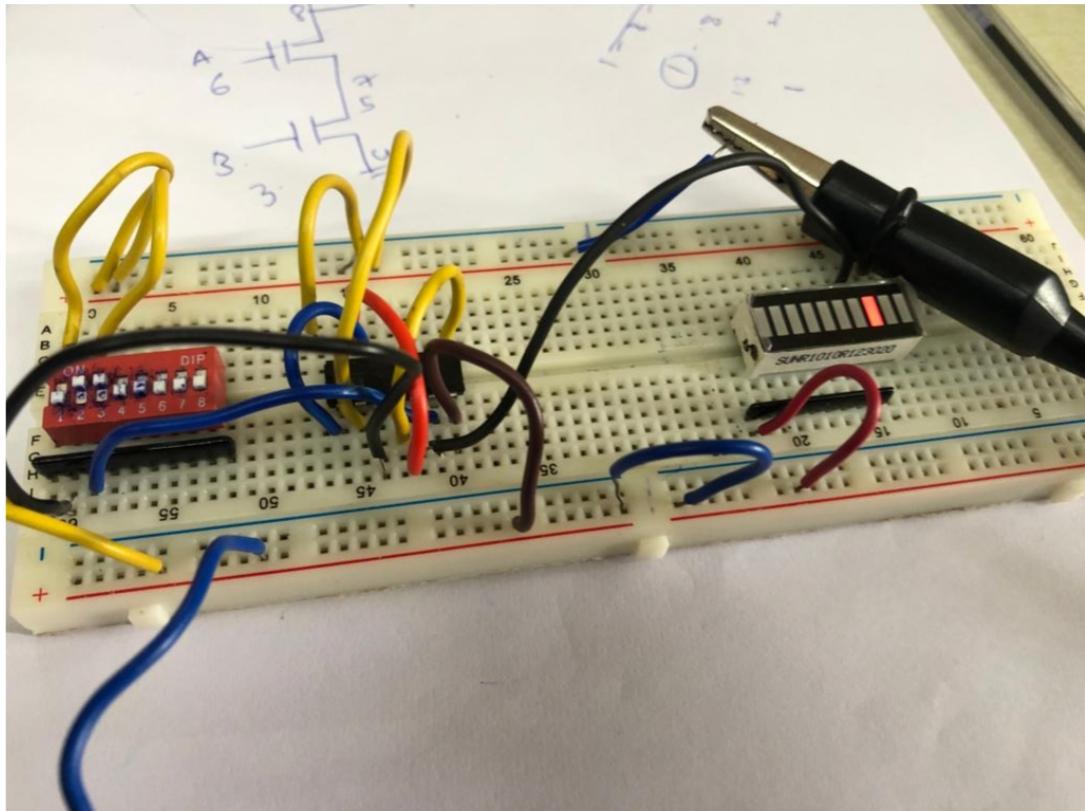

Results and Discussions:

We have implemented the AND and XOR gates using the CMOS logic gates using HCF 4007's, and have solved the problems 1 & 2 and also implemented all the other logic gates – NOR, OR, NAND, XNOR using CMOS logic gates.

Conclusion:

Logic gates for the given problems are XOR and AND respectively and we have implemented them and all other gates using the CMOS logic gates.