

## Experiment No. 8

### Non- Ideal characteristics of Op Amp Circuits

#### Objectives:

Measurement of Offset Voltage, Bias Currents, Slew rate and Open-loop Gain of Op-Amps

#### Equipment/Components Required:

1. Op-Amp  $\mu A$  741
2. Resistors –  $100\ \Omega$
3. Regulated Power Supply
4. Variable Power Supply
5. Multimeter
6. Digital Storage Oscilloscope
7. Arbitrary Function Generator

#### Steps:

##### Part A: Input offset voltage

1. Wire up the circuit as shown in Figure 1. Let  $R_1=R_2=10k\Omega$ .
2. Measure the values of the resistors using multimeter.
3. Measure the output Voltage,  $V_o$ .

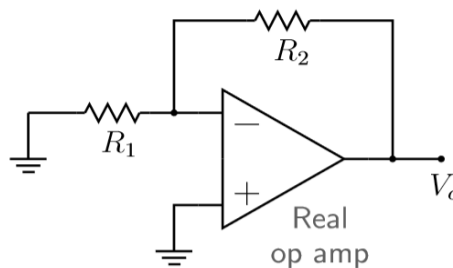


Figure 1: Offset voltage measurement

4. The Offset voltage,  $V_{os}$  is calculated as:

$$V_{os} = \frac{V_o}{A_v}$$

## Part B: Offset current measurement

1. First wire up the circuit as shown in Figure 2 (a).

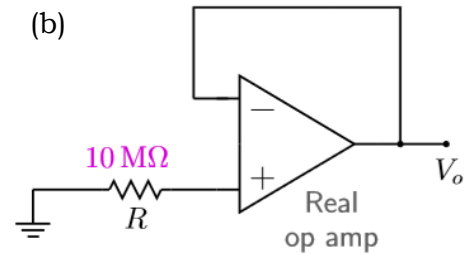
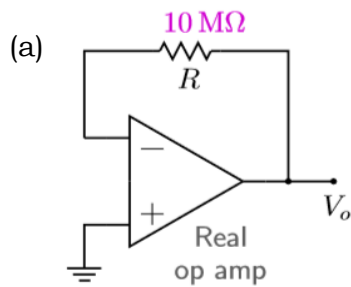


Figure 2: Circuits for Offset current measurement (a)  $I_{B^-}$  (b)  $I_{B^+}$

2. Measure the output voltage,  $V_o$ .

3. Now connect the circuit as shown in Figure 2(b) and measure the output voltage.

4. Fill-in your observations and calculate the input bias current,  $I_B$  and offset current,  $I_{OS}$  using the formulae given in the table

$V_o$ (V)	$I_{B^-} = \frac{V_o}{R}$	$I_{B^+} = \frac{V_o}{R}$	$I_B = (I_{B^-} + I_{B^+})$	$I_{OS} =  I_{B^+} - I_{B^-} $

## Part C: Slew rate and Bandwidth measurement

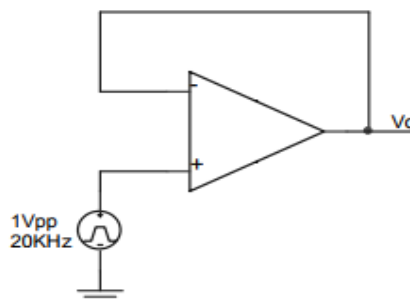


Figure 3: Circuit for Slew rate measurement

1. Connect the circuit of Figure 3.

2. Using a function generator, provide a 1V peak-to-peak square wave with a frequency of 25 KHz.

3. With an oscilloscope, observe the output of Op-Amp. Adjust the oscilloscope timing to get a couple of cycles.

4. Measure the voltage change during rising edge and the falling edge of the output voltage,  $\Delta V$ .
5. Note the change in time change,  $\Delta T$  for which  $\Delta V$  occurs in the output waveform.
6. Calculate the slew rate using the formula  $SR = \Delta V / \Delta T$ .

Sl. No	Frequency	$\Delta V$	$\Delta T$	$SR = \Delta V / \Delta T$

#### Part D: Bandwidth measurement

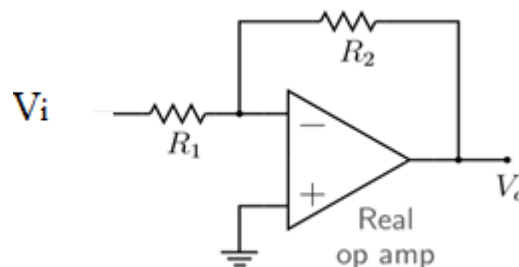


Figure 4: Bandwidth measurement

1. Connect the circuit of Figure 4.
2. Using a function generator, provide a 1V peak-to-peak sine wave.
3. Vary the frequency from 1 kHz to 500 kHz and note down the corresponding gain.
4. Measure the bandwidth when gain falls below 3dB.

**$V_i = 1V_{p-p}$ ,  $R_1 = R_2 = 10\text{ k}\Omega$**

Sl. No.	Frequency	Gain

**Bandwidth = \_\_\_\_\_**

### Part E: Measurement of DC open-loop gain

One of the most important features of an op amp is a high open-loop gain  $A_{OL}$  that is typically in the range  $10^5$  to  $10^6$ . Measurement of  $A_{OL}$  with a simple scheme shown in Figure 5 does not work for the following reasons:

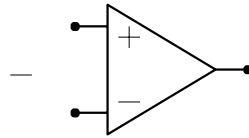


Figure 5: An op amp operated in the open-loop configuration.

(a) With a large gain of  $10^5$  or more, the op amp is likely to be driven to saturation because of the input offset voltage  $V_{OS}$  which is typically in the range  $-5\text{mV}$  to  $+5\text{mV}$  for Op Amp 741.

(b) Even if we had a magical op amp with  $V_{OS} = 0\text{V}$  (or we compensated for the effect of  $V_{OS}$  by some means), measurement of  $A_{OL}$  is still a challenge. Suppose  $A_{OL} = 2 \times 10^5$ , and we want an output voltage of  $1\text{V}$ , for example. This would require  $V_i = 1\text{V} / 2 \times 10^5 = 5\mu\text{V}$ , a very small voltage to apply or measure in the lab.

Given the above difficulties, how do we reliably measure  $V_{OL}$ ? The trick is to use the op amp in a “servo loop” which ensures that its input voltage remains small enough to keep it in the linear region. The op amp for which we want to measure  $A_{OL}$  is marked in the figure 6 as the Device under Test (DUT). The circuit has a high overall gain, but because of the negative feedback provided by  $R_3$ , it is stable. The capacitor  $C$  prevents the circuit from oscillating. We can measure the open-loop gain  $A_{OL}$  of the DUT using the following steps.

1. Using the  $10\text{k}$  pot, first nullify the effect of the offset voltage of the DUT to the extent possible, i.e., adjust the pot, with the switch in position 1 (or simply open), to make  $V_o$  as small as possible. Let us use  $V_{A_o}$  and  $V_{A_{o1}}$  to denote the values of  $V_o$  and  $V_{o1}$ , respectively.
2. Now change the switch to position 2. With  $V_{(2)-} \approx V_{(2)+} = 0\text{V}$  and with the capacitor behaving like an open circuit in the DC condition, we have  $i_1 = i_2$ , and

