

# **LAB REPORT-5**

MOS differential amplifier

MIRIYALA PRANAY KAMAL

200030033


P NITIN SRINIVAS

200030042

## **NMOS current mirror**

Q4.  $I_{DS}$  for different values of  $V_{DS}$ :

NMOS current mirror	
$V_{ds}$	$I_{ds}$
0.122	0.57
0.2	1
0.3	1.52
0.4	2.03
0.5	2.49
0.6	2.9
0.7	3.39
0.8	3.86
1	4.74
1.1	5.16
1.2	5.5
1.3	5.78
1.4	6.3
1.5	6.56
1.7	7.55
1.8	7.78
1.9	8.25
2	8.5
4.3	11.9
5.83	13.1
6.2	13.22
7.35	13.24
9.18	13.96
10.83	13.53
11.73	14.36

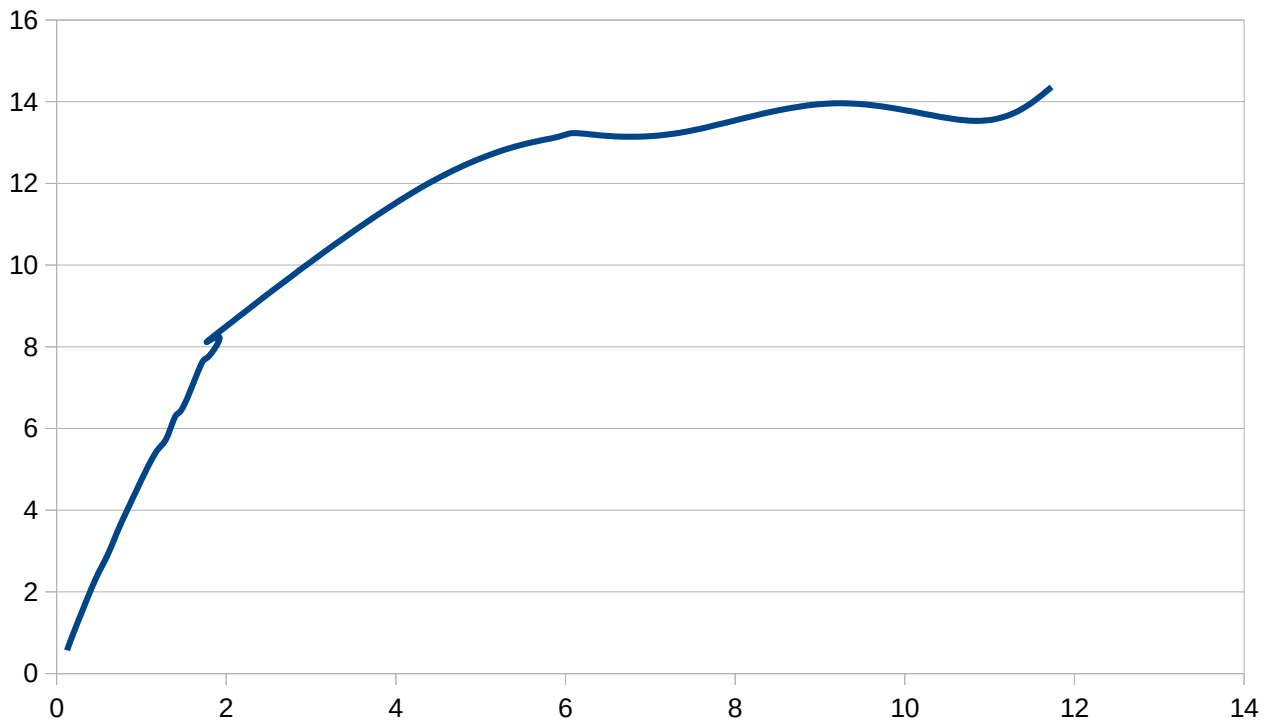

For smaller values of  $V_{DS}$ , the MOSFET will be in triode region, whereas as  $V_{DS}$  increases,  $I_{DS}$  begins to saturate and operates in saturation region.

Q5. The output impedance of the current mirror is simply found from the slope of  $I_{DS}$  vs  $V_{DS}$  in the saturation region.

$$R_o = \frac{1}{\text{Slope}} = \frac{7.35 - 6.2}{13.24 - 13.22} \times 10^3 = 57.5 \text{ k}\Omega$$

We know that, channel length modulation parameter ( $\lambda$ ) and  $R_o$  are related by

$$R_o = 1/(\lambda \times I_{DS})$$

Here,  $I_{DS}$  is the saturated value of current in the absence of channel length modulation, which from the plot is 13.56 mA.

So, channel length modulation parameter ( $\lambda$ ) will be,

$$\lambda = \frac{1}{(R_o \times I_{DS})} = \frac{1}{57.5 \text{ k}\Omega \times 13.56 \text{ mA}} = 0.0128 \text{ V}^{-1}$$

### **CMOS differential amplifier**

Q2.Values of  $R_1$  and  $C_i$  for a lower cut-off frequency  $<30$  Hz are:

$$R_1 = 2.4 \text{ k}\Omega$$

$$C_i = 2.2 \text{ }\mu\text{F}$$

Q3.The Frequency response of the amplifier by varying the frequency from 10 Hz to 100 MHz

Frequency(in Hz)	$V_i$ ( $V_{p-p}$ in mV)	$V_o$ ( $V_{p-p}$ in V)	Phase difference
100	100	2.1	50
500	100	2.1	15
1000	100	2.1	15
2000	100	2.2	10
5000	100	2.2	5
7000	100	2.2	0
10000	100	2.2	0
15000	100	2.2	-5
25000	100	2.1	-10
35000	100	1.8	-30
40000	100	1.7	-45
50000	100	1.6	-45
100000	100	1	-60
500000	100	0.8	-85
1000000	100	0.5	-100
10000000	100	0.5	-100

Q7.The Frequency response of the amplifier by varying the frequency from 10 Hz to 100 MHz for the modified circuit:

Frequency(in Hz)	$V_i$ ( $V_{p-p}$ in mV)	$V_o$ ( $V_{p-p}$ in V)	Phase difference
100	30	1	30
500	30	1	20
1000	30	1	0
2000	30	1	0
5000	30	1	-5
7000	30	1	-10
10000	30	1	-15
15000	30	1	-20
25000	30	1	-30
35000	30	0.9	-50
40000	30	0.8	-60
50000	30	0.7	-85
100000	30	0.4	-100
500000	30	0.3	-100
1000000	30	0.2	-100
10000000	30	0.2	-100

#### Discussion:

1. I understood how to implement a NMOS Common Source Amplifier and found out the required resistances  $R_2$  and  $R_D$  that need to be implemented in the circuit for the CMOS to work in amplifier mode.
2. Understood the frequency dependent amplification nature of the NMOS Common Source Amplifier.
3. Operation of Arbitrary Function Generator (AFG) and Digital Oscilloscope for generation and analysis of Periodic signals at different frequencies and finding out the gain of the signal for various frequencies and various input voltages.
4. As the frequency of the input sinusoid increases from 30 Hz to 100 MHz, initially, the gain increases becomes almost constant in the mid-band frequency range and after that starts decreasing.
5. Since The active region in  $I_{ds}$  vs  $V_{gs}$  curve of MOSFET resemble a line for small values of  $V_{gs}$ , It will not Be linear but approximately parabolic for large values of  $V_{gs}$  and that is why we are having distortions for large amplitude input waves while increasing amplitude of Input sine wave.
6. All our Simulation and Hardware Results are Similar, so we have successfully understood how to use MOS based amplifiers.

