 


1. Write a structural style VHDL code for a 4bit adder/subtractor. The 4bit adder/subtractor comprises of 1 bit full adders. Use suitable switches for inputs and LEDs for outputs in the CPLD board.



----- VHDL CODE FOR 4_BIT ADDER_SUBTRACTOR WITH CONTROL SIGNAL-----

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
--define the entity with ports
```

```
entity adsub_4bit is
```

```
Port ( a : in STD_LOGIC_VECTOR (3 downto 0);
```

```
);
```

```
end adsub_4bit;
```

-----DEFINE THE ARCHITECTURE FOR ADDER_SUBTRACTOR

```
architecture rtl of adsub_4bit is
```

```
--DEFINE THE COMPONENT FULL ADDER USED-----
```

```
--DEFINE THE INTERMEDIATE SIGNALS IF REQUIRED-----  
--DEFINE THE FUNCTIONALITY WITH STRUCTURAL MODELING--  
begin  
end rtl;
```


-----VHDL CODE FOR 1 bit full adder-----

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
--Define input and output ports  
entity fulladder is  
Port ( x : in STD_LOGIC;  
y : in STD_LOGIC;  
z : in STD_LOGIC;  
sum : out STD_LOGIC;  
cout : out STD_LOGIC);  
end fulladder;
```

```
--Defining the architecture of full adder in dataflow modelling style  
architecture b_fa of fulladder is  
begin  
sum =x xor y xor z;  
cout = (x and y) or (x and z) or (y and z);  
end b_fa;
```


2. Write a behavioural style VHDL code for an ALU described below.

Select inputs	ALU operation
00	A+B
01	A-B
10	A and B
11	A xor B

 

-----VHDL CODE FOR 3-BIT ALU-----

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

use ieee.NUMERIC_STD.all; ----- *USED FOR ARITHMETIC COMPUTATIONS.*

-----DECLARE THE ENTITY-----

entity ALU is

Port (

A, B : in STD_LOGIC_VECTOR(2 downto 0); -- 2 inputs 3-bit

--- *ENTER THE REMAING PORTS*-----

);

end ALU;

----- *WRITE THE ARCHITECTURE IN BEHAVIOURAL MODELLING STYLE WITH
CONDITIONAL STATEMENTS*-----

architecture Behavioral_ALU of ALU is

-----*DECLARE THE SIGNALS IF REQUIRED*-----

begin

end Behavioral_ALU;