

# Lab-2 Report

Implementation of CMOS logic gates

MIRIYALA PRANAY KAMAL  
200030033

**Aim:** Identification of logic gates required for the given problems and implementation of the problem using the CMOS logic gates.

## Components used:

1. IC HCF 4007 CMOS gates
2. Resistor array
3. DIP switches
4. LED displays
5. Breadboard
6. Power supply
7. Multimeter

## Design Procedure:

### **Problem Statements:**

1. A bulb in a staircase has two switches, one switch being at the ground floor and the other one at the first floor. The bulb can be turned ON and also can be turned OFF only if both the switches are at different states. Design the CMOS circuit for this logic.

Solution: **XOR Gate.**

2. A commercial building is powered by two renewable sources of energy – solar and wind. There are two alarms associated to both the generation stations that get HIGH if the power generation in any day is below the threshold values. Design the CMOS circuit that implements the logic of a third alarm which is switched ON if the generation by both the sources are below threshold on any given day.

Solution: **AND Gate.**

These XOR and AND gates can be implemented by using CMOS IC HCF 4007. The logic tables/Truth tables for these gates are:

## AND GATE


INPUT 1	INPUT 2	OUTPUT
0	0	0
0	1	0
1	0	0
1	1	1

## XOR GATE


INPUT 1	INPUT 2	OUTPUT
0	0	0
0	1	1
1	0	1
1	1	0

Circuit diagram:

## AND GATE USING CMOS

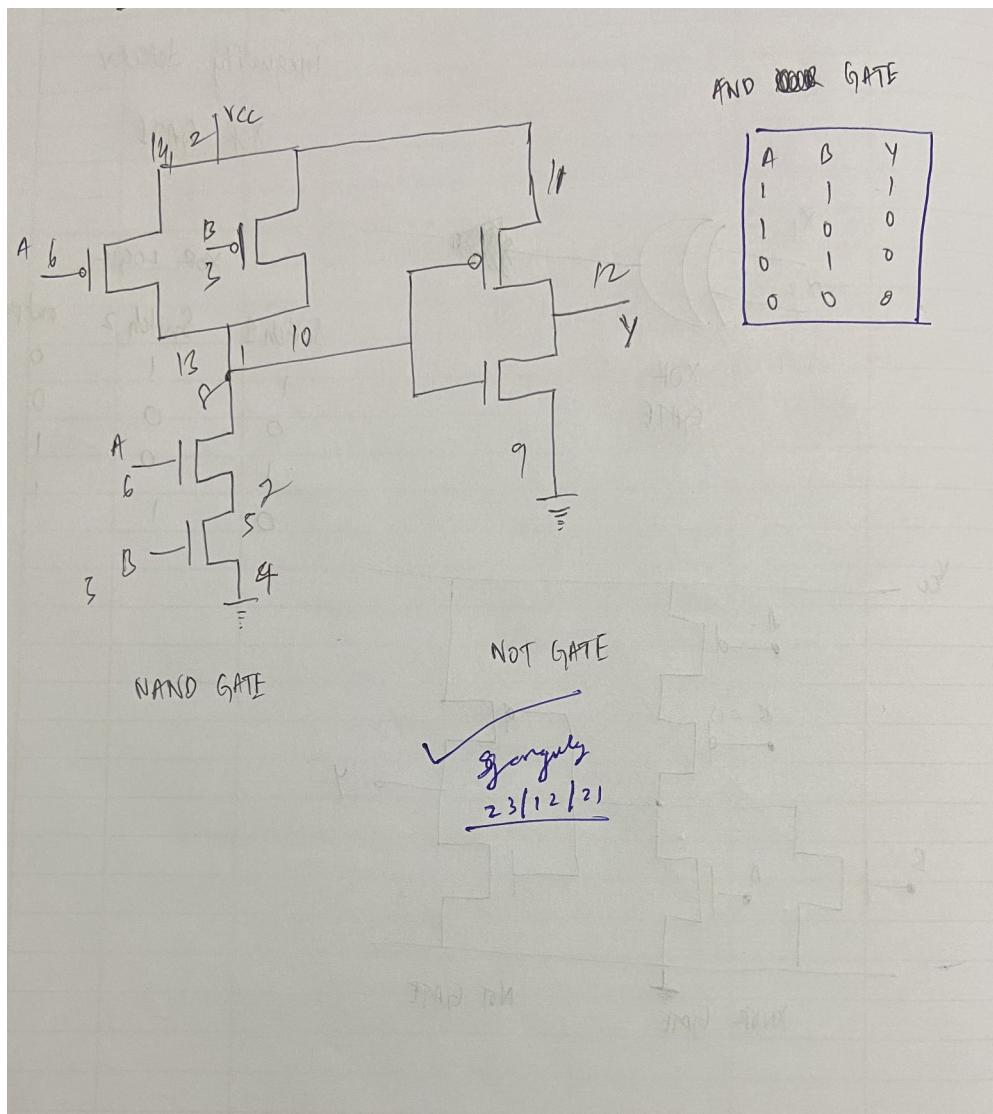


## XOR GATE USING CMOS

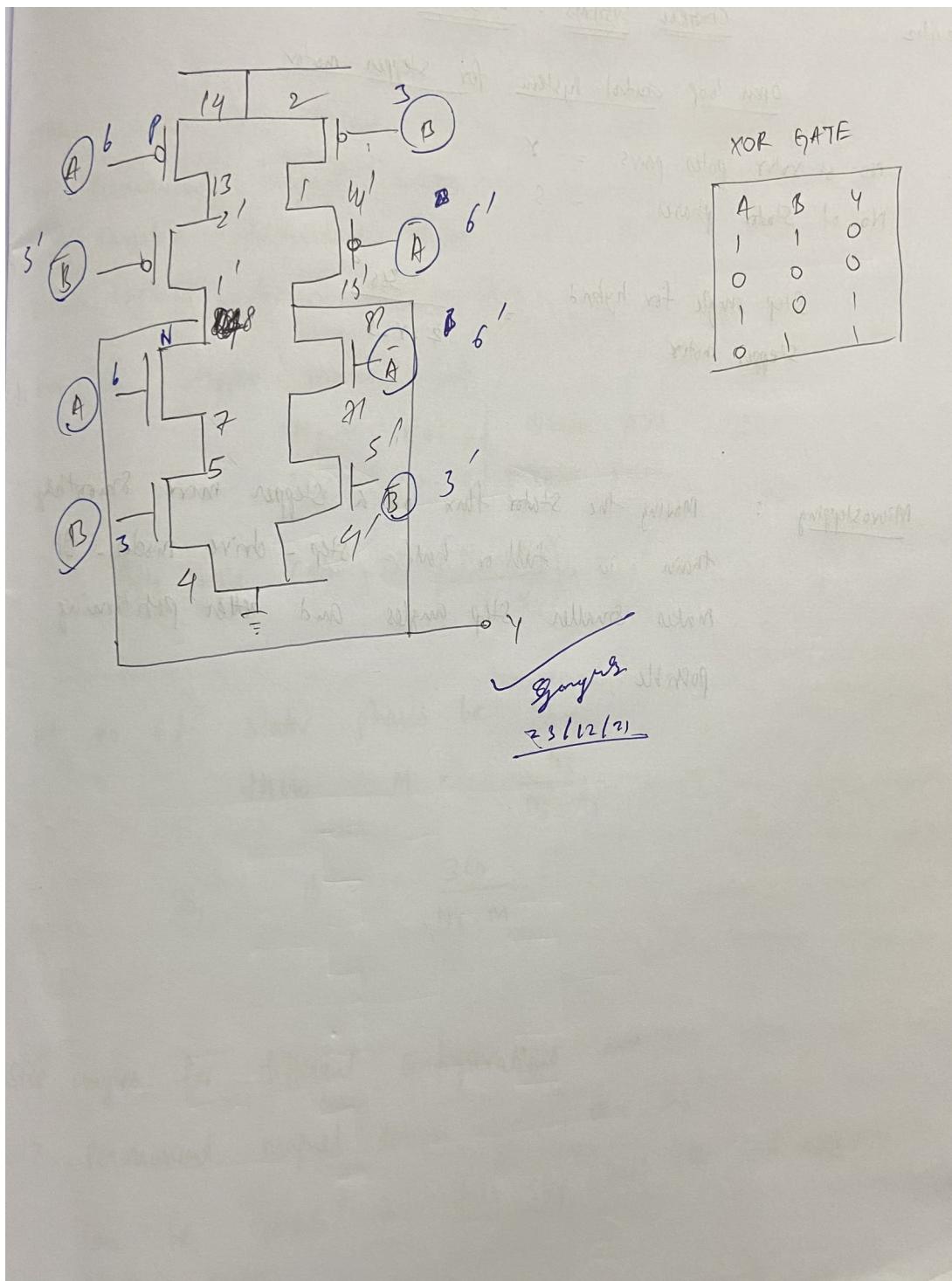



## Circuit Snapshots:

### **1. XOR GATE**

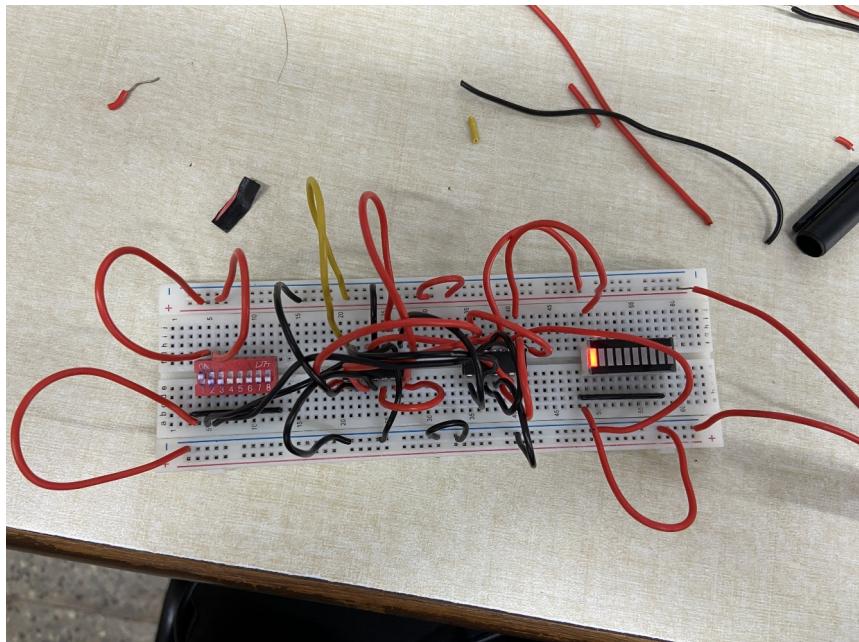

### **2. AND GATE**

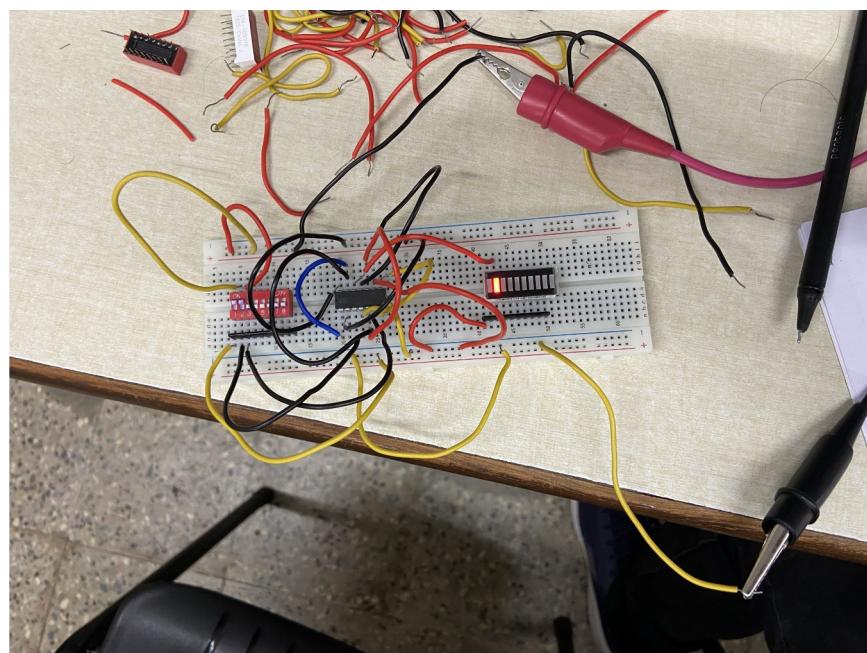

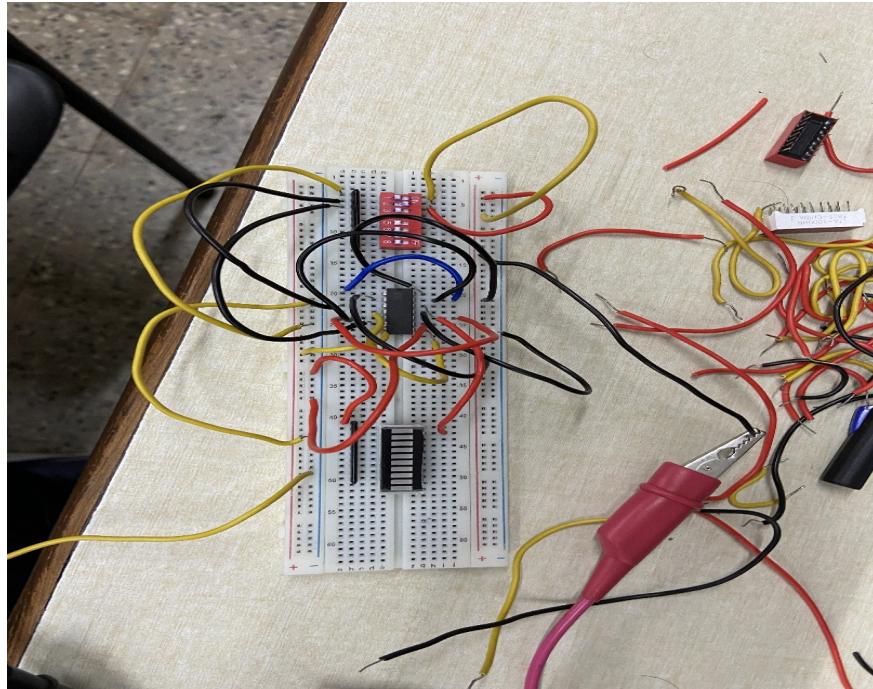

## **Results and Discussions:**

We have implemented the AND and XOR gates using the CMOS logic gates using HCF 4007's, and have solved the problems 1 & 2.

## **Conclusion:**

Logic gates for the given problems are XOR and AND respectively and we have implemented them using the CMOS logic gates.