

[illegible]

Hardware Exercise Objectives:

1. To study the different types of DC Biasing for a BJT Common-Emitter Amplifier
2. To find the effect of the biasing schemes on stability factor (dI_C/dV_{BE})

Equipment/Components Required:

1. BJT – 2N2222
2. Resistors – $100\ \Omega$
3. Regulated Power Supply
4. Variable Power Supply
5. Multimeters – 2Nos

Steps:

1. Wire up the circuit as shown in Figure 2 (a). Make sure that the BJT is operating in active region.



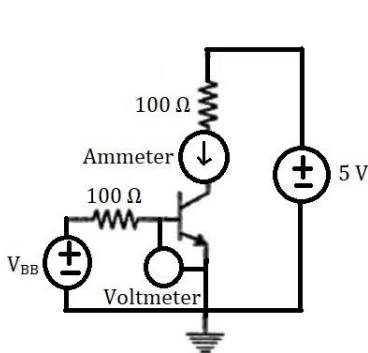


Figure 2(a): Fixed Bias

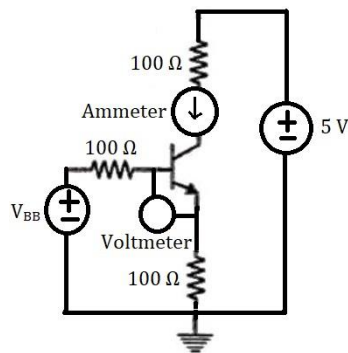

2(b): Self-Bias

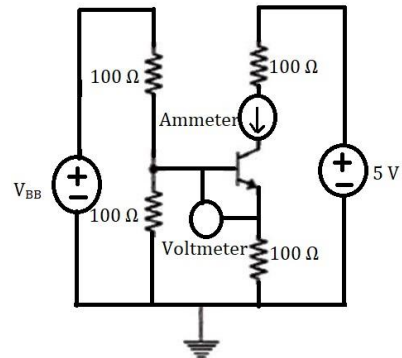

2(c): Potential-Divider Bias

2. Vary the voltage V_{BB} in steps of 0.2 V. Make sure that the BJT keeps operating in active region.
3. Note down the values of V_{BE} (using the voltmeter) and I_C (using the ammeter) for different V_{BB} .
4. Repeat steps 2 and 3 for self-bias (Figure 2(b)) and potential-divider bias (Figure 2(c)) circuits.
5. Calculate the values of dI_C/dV_{BE} for all the three circuits.
6. Which circuit is better and why?