

LAB REPORT -3

BJT Common Emitter Amplifier Characteristics

MIRIYALA PRANAY KAMAL

200030033

P NITIN SRINIVAS

200030042

Q2. Net list for the circuit :

BJT Common Emitter Amplifier Characteristics

Vcc 4 0 12

R1 4 5 36k

R2 5 0 10k

Rc 4 7 5k

Re 3 8 1.99k

vdc 7 1 dc=0

vde 8 0 dc=0

vdb 5 2 dc=0

Q1 1 2 3 Q2N2222A

.model Q2N2222A NPN(IS=8.11E-14 BF=205 VAF=113 IKF=0.5 ISE=1.06E-11 NE=2 BR=4
VAR=24 IKR=0.225 RB=1.37 RE=0.343 RC=0.137 CJE=2.95E-11 TF=3.97E-10 CJC=1.52E-
11 TR=8.5E-8 XTB=1.5)

Q3. Values of V_{CE} , I_C , I_E , I_B , V_E obtained are:

No. of Data Rows : 2				
bjt common emitter amplifier characteristics				
DC transfer characteristic Thu Dec 30 11:49:09 2021				
Index	v-sweep	v(1,3)	v(3)	
0	0.000000e+00	-9.50284e-25	9.560875e-25	
1	1.200000e+01	5.137738e+00	1.962002e+00	
bjt common emitter amplifier characteristics				
DC transfer characteristic Thu Dec 30 11:49:09 2021				
Index	v-sweep	i(vdc)	i(vdb)	i(vde)
0	0.000000e+00	-1.16064e-30	4.816066e-28	4.804460e-28
1	1.200000e+01	9.800520e-04	5.878563e-06	9.859306e-04
ngspice 6 ->				

- $V_{CE} = 5.13 \text{ V}$
- $V_E = 1.96 \text{ V}$
- $I_C = 0.98 \text{ mA}$
- $I_E = 5.87 \mu\text{A}$
- $I_B = 0.985 \text{ Ma}$

Q4. Values of C_B , C_C , C_E for the signal frequency of 2 kHz to be in the mid-band region are:

$$C_B = 2.03 \mu\text{F}$$

$$C_C = 3.1 \mu\text{F}$$

$$C_E = 7.99 \mu\text{F}$$

Frequency response will look like:

BJT Common Emitter Amplifier Characteristics

vin 8 0 dc=0 ac=100m

vcc 1 0 dc=12

vdc 6 3

vde 7 8

vdb 2 4

r1 1 2 36.08k

r2 2 0 10k

rc 1 6 5k

re 5 7 1.99k

rl 9 0 1k

q1 3 4 5 Q2N2222A

cb 2 8 2.03u

cc 6 9 3.1u

ce 5 0 7.99u

.model Q2N2222A NPN(IS=8.11E-14 BF=205 VAF=113 IKF=0.5 ISE=1.06E-11 NE=2 BR=4
VAR=24 IKR=0.225 RB=1.37 RE=0.343 RC=0.137 CJE=2.95E-11 TF=3.97E-10 CJC=1.52E-
11 TR=8.5E-8 XTB=1.5)

.ac dec 1000 100 100G

*Control Statements


.control

run

plot vdb(9) xlog

.endc

.end

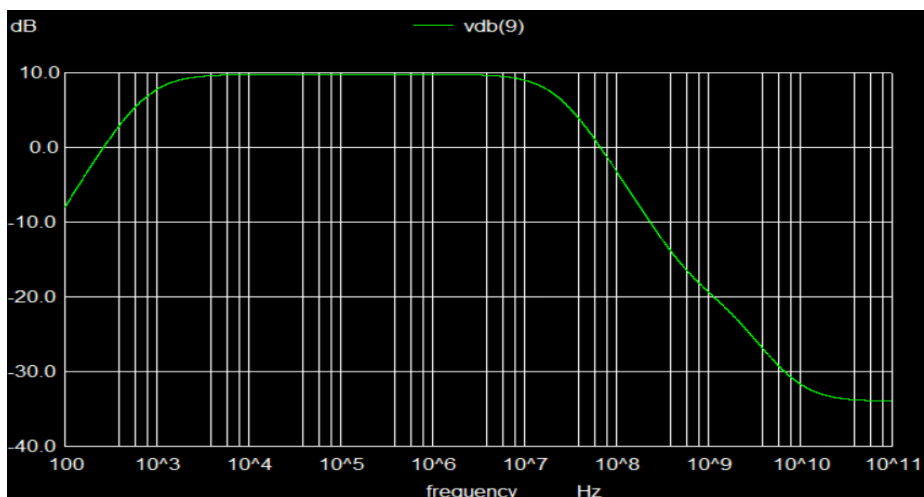

Q5. Output voltage waveform and input voltage waveform

BJT Common Emitter Amplifier Characteristics

```
vin 8 0 sin(0 0.01 2000)
```

```
vcc 1 0 dc=12
```

```
vdc 6 3
```

```
vde 7 8
```

```
vdb 2 4
```

```
r1 1 2 36.08k
```

```
r2 2 0 10k
```

```
rc 1 6 5k
```

```
re 5 7 1.99k
```

```
rl 9 0 1k
```

```
q1 3 4 5 Q2N2222A
```

```
cb 2 8 2.03u
```

```
cc 6 9 3.1u
```

```
ce 5 0 7.99u
```

```
.model Q2N2222A NPN(IS=8.11E-14 BF=205 VAF=113 IKF=0.5 ISE=1.06E-11 NE=2 BR=4  
VAR=24 IKR=0.225 RB=1.37 RE=0.343 RC=0.137 CJE=2.95E-11 TF=3.97E-10 CJC=1.52E-  
11 TR=8.5E-8 XTB=1.5)
```

```
.tran 0.002ms 6ms
```

```
*Control Statements
```


```
.control
```

```
run
```

```
plot v(9) v(8)
```

```
.endc
```

```
.end
```

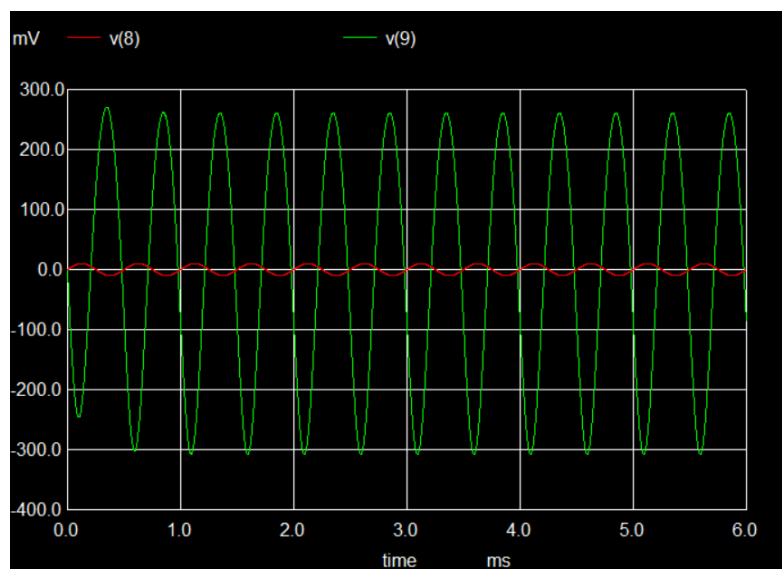


Hardware Exercise

Amplitude of the sinusoidal input = 200 mV_{p-p}

Varying the frequency from 100 Hz to 1.5 MHz gives us:

<u>Frequency(in Hz)</u>	<u>V_{out} for 100mV pp</u>	<u>V_{out} for 500mV pp</u>	<u>V_{out} for 1v</u>
100	9.1	9.8	10.5
500	9.7	11.5	12.7
1000	10.1	12.2	12.9
2000	10.9	12.7	13
5000	11.3	12.8	13.1
10000	11.5	12.8	13.1
20000	11.6	12.8	13
50000	11.6	12.8	12.9
100k	11.6	12.7	12.8
500k	11.6	12.4	12.3
750k	11.3	12.2	12.2
1m	11.1	11.9	12
1.1m	10.9	11.7	11.9
1.2m	10.7	11.7	11.8
1.4m	10.6	11.4	11.6
1.5m	10.6	11.4	11.5
2m	10.2	10.9	11

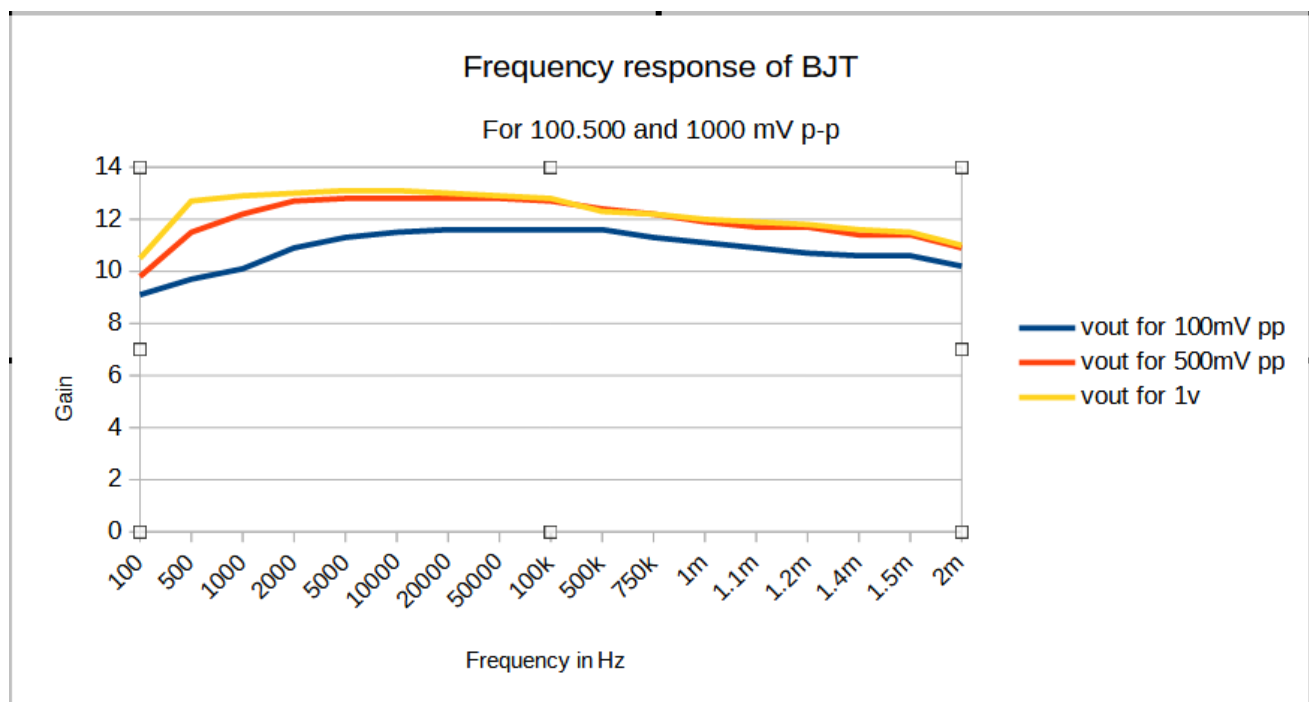

The gain is constant over a range of frequencies and increases and decreases before and after the range of frequencies.

After increasing the input amplitude to 500 mVp-p and 1Vp-p the output signal is clipped and clipping is prominently observed at higher voltages.

Discussion:

1. I understood how to implement a BJT circuit into a common emitter mode amplifier and found out the required resistances that need to be implemented in the circuit for the BJT to work as an amplifier.

BJT Common Emitter Amplifier

$V_{CE} = 5V$
 $V_C = 5V + V_E = 7V$
 $R_2 = 10k\Omega$
 $R_C = \frac{V_{CC} - V_C}{I_{mA}} = \frac{5V}{1mA} = 5k\Omega$

$\beta = 205$ from model for BJT 2N2222A.

So, $\frac{I_C}{I_B} = 205 \Rightarrow I_B = \frac{1mA}{205} = 4.87 \times 10^{-6}A$

$I_E = I_C + I_B = 1.0048mA$

Also, $I_S = 8.11 \times 10^{-14}$ from BJT model, $V_T = 26mV$ (from BJT equation)

So, $I_C = 8.11 \times 10^{-14} \cdot e^{V_{BE}/26 \times 10^{-3}}$

$1 \times 10^{-3} = 8.11 \times 10^{-14} \cdot e^{V_{BE}/26 \times 10^{-3}}$

$V_{BE} = (26 \times 10^{-3}) \left(\ln \left(\frac{10^{-3}}{8.11} \right) \right) = 0.604118V$

So, $V_B = V_{BE} + V_E = 0.604 + 2 = 2.604V$

By using KCL at base,

$$\frac{12 - 2.604}{R_1} = \frac{2.604}{10 \times 10^3}$$

$$R_1 = 36.082k\Omega$$

Similarly, $R_E = \frac{2V}{1.0048mA} = 1.99k\Omega$

2. Understood the frequency dependent amplification nature of the BJT CE amplifier and also adjusting the mid band range of frequencies by varying the capacitance values at emitter, base and collector regions of the BJT.
3. Operation of Arbitrary Function Generator (AFG) and Digital Oscilloscope for generation and analysis of Periodic signals at different frequencies.