

# Experiment-1

## Light Emitting Diode Characterizations

### Simulation Exercise

1. Write an ngpice netlist to measure I/V characteristics of RED, GREEN and BLUE LEDs.
2. Run the simulation and plot all the characteristics on the same plot. Call this Plot 1.
3. Now plot a graph of  $\ln I_D$  v/s  $V_D$  for all the diodes. Call this Plot 2. The slope of the graph is given by

$$\frac{\ln I_{D2} - \ln I_{D1}}{V_{D2} - V_{D1}} = \frac{1}{\eta V_T} \quad (1)$$

Calculate the ideality factor  $\eta$  of each diode from the slope. Also calculate the saturation current  $I_s$  from the y-intercept.

4. Calculate the bandgap  $E_g$  for each LED using the emission wavelengths as:

$$E_g = \frac{1240}{\lambda} \quad (2)$$

5. From Plot 1, find the cut-in voltage,  $V_0$  for each of the LED.
6. Now plot a graph of  $V_0$  v/s  $E_g$  for all the diodes. Hence you can plot all three points (for the different diodes) on a single graph.

### Hardware Exercise Objectives:

1. To characterize the different LEDs.
2. To identify the band gap of LEDs

### Equipment/Components Required:

1. LEDs – Red, Green, Blue,
2. Resistor – 1k $\Omega$
3. Variable power supply
4. Multimeters – one ammeter and a voltmeter

### Steps:

1. Make the circuit connections as shown in Figure 1.

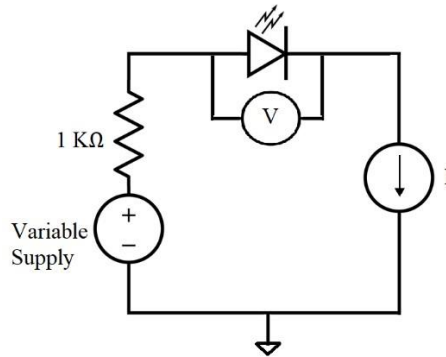


Figure 1

2. Vary the supply voltage from 0 – 5V in steps of 0.2 V and measure the  $V_D$  and  $I_D$ .
3. Tabulate your observations and plot  $I_D$  Vs  $V_D$ . Name this plot 3.
4. Now plot a graph of  $\ln I_D$  Vs  $V_D$ . Call this plot as plot 4. Calculate the ideality factor  $\eta$  from the slope and the saturation current  $I_s$  from the y - intercept for the given diode.
5. Repeat steps 2 to 4 for all the three LEDs.
6. Are the hardware observations same as simulation results?
7. Plot the cut-in voltage Vs  $E_g$  for all the three diodes.
8. Calculate the reverse saturation current of each LED using equation.

$$I_D = I_{00} e^{-\frac{E_g}{kT}} \left( e^{\frac{qV_D}{kT}} - 1 \right)$$