

## Experiment No. 9

### Active Filters

#### Objectives:

To understand the characteristics of low-pass, high pass, band pass and band stop active filters

#### Equipment/Components Required:

1. Op-Amp  $\mu A 741$
2. Resistors
3. Capacitors
4. Regulated Power Supply
5. Digital Storage Oscilloscope
6. Arbitrary Function Generator

#### Steps:

1. Compute the cut off frequency of LPF, HPF and the band stop filter shown in Figure 1 with  $R_a = 8\text{ k}\Omega$ ,  $R_b = 2.2\text{ k}\Omega$ ,  $R_1 = R_F = 1\text{ k}\Omega$ ,  $C_a = C_b = 10\text{ nF}$ .

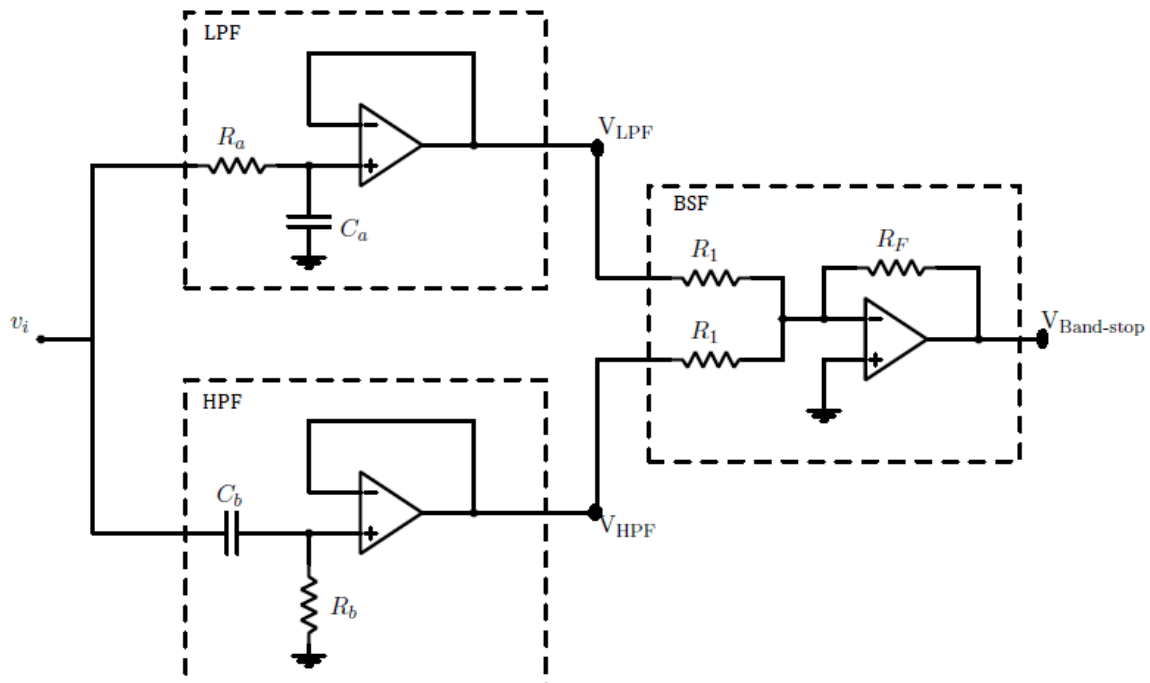


Figure 1: Circuit for Active Filters

2. Connect the circuit of the band-stop filter as shown in Figure 1. This circuit includes sub-circuits of a high pass filter, a low pass filter and an adder.

3. Apply a sinusoidal input having amplitude 100 mV, vary the frequency from 100 Hz to 100 KHz and observe the output of the low pass, high pass and band-pass outputs.

4. Plot the magnitude and phase response of all the three filters.

Freq.	$V_i$ (V <sub>p-p</sub> V)	$V_o$ (V <sub>p-p</sub> V)	Phase diff.

### Band pass filter

- Compute the cut-off frequencies of the band pass filter shown in Figure 2. Given  $R_a=2.2\text{ k}\Omega$ ,  $R_b=22\text{ k}\Omega$  and  $C_a=C_b=10\text{ nF}$ .

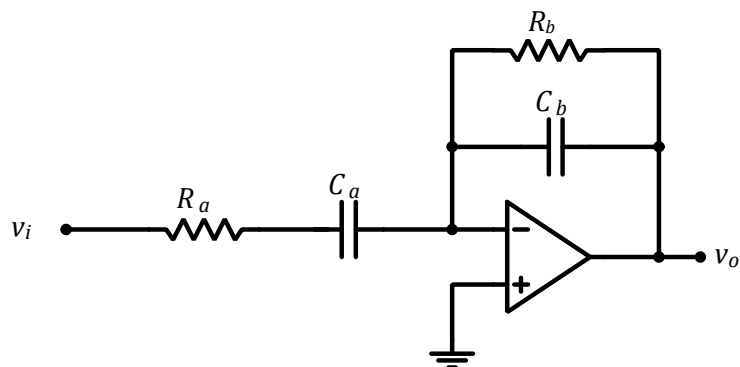


Figure 2: Circuit for a band-pass active filter.

- Apply a sinusoidal input having amplitude 100 mV, vary the frequency from 100 Hz to 100 kHz and observe the output.

- Plot the magnitude and phase response of the filter.

### Band pass filter

[illegible]